
Sequence 110

X02122_en

Design a sequential circuit with one binary input and one binary output. The output must be 1 at cycle i when the inputs at cycles $i - 2$, $i - 1$ and i are 110, otherwise the output must be 0.

The top module must be called *find110*.

```
module find110(in, out, clk, rst );  
    input in, clk, rst ;  
    output out;
```

Hint

The state machine can be implemented with 3 states.

Input

- *clk* is the clock signal
- *rst* is the synchronous reset signal.
- *in* is the binary input.

Output

- *out* is the output that behaves according to the specification.

Problem information

Author : Jordi Cortadella

Generation : 2013-07-17 16:32:31

© Jutge.org, 2006–2013.

<http://www.jutge.org>