
Heating-cooling system

X04334_en

Design a circuit that controls a heating-cooling system. The system has two sensors that indicate when the temperature is too high (*hot*=1) or too cold (*cold*=1). The sensors will never be at 1 simultaneously.

If the temperature is too hot, the cooler must be activated (*cooler*=1). If the temperature is too cold, the heater must be activated (*heater*=1).

Specification

```
module heater_cooler (hot, cold, heater, cooler);  
  input hot, cold;  
  output heater, cooler;
```

Input

- *hot* is the input that indicates when the temperature is too hot.
- *cold* is the input that indicates when the temperature is too cold.

Output

- *heater* is the output that activates the heater.
- *cooler* is the output that activates the cooler.

Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:58:52

© Jutge.org, 2006–2013.

<http://www.jutge.org>