

---

## Simple state machine

X52189\_en

---

Design a sequential network described by the following state/output table (*PS*: Present State; *NS*: Next state, *z* is the 2-bit output). Assume *A* is the initial state and encode the outputs as  $a = 00$ ,  $b = 01$  and  $c = 10$ .

<i>PS</i>	Input	
	$x = 0$	$x = 1$
<i>A</i>	<i>B, a</i>	<i>F, b</i>
<i>B</i>	<i>C, a</i>	<i>A, c</i>
<i>C</i>	<i>D, a</i>	<i>B, b</i>
<i>D</i>	<i>E, b</i>	<i>C, c</i>
<i>E</i>	<i>F, b</i>	<i>D, b</i>
<i>F</i>	<i>A, c</i>	<i>E, c</i>
	<i>NS, z</i>	

### Specification

```
module state_machine(x, z, clk, rst );
    input x, clk, rst ;
    output [1:0] z;
```

### Input

- *clk* is the clock signal.
- *rst* is the synchronous reset signal.
- *x* is the input signal.

### Output

- *z* is the 2-bit signal encoding the outputs *a*, *b* and *c*.

### Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:57:16

© Jutge.org, 2006–2013.

<http://www.jutge.org>