
4-bit comparator

X61860_en

Design a circuit that compares two 4-bit numbers represented in binary code and indicates whether the first is greater than, equal to or smaller than the second.

The root module must be called *cmp4*.

```
module cmp4(a, b, eq, gt, lt );  
    input [3:0] a, b;  
    output eq, gt, lt ;
```

Hint

Design a 1-bit comparator that receives the result of the comparison of the least-significant bits. Use four instances of this circuit.

Input

- *a* and *b* are the two 4-bit input numbers.

Output

- *eq* indicates that $a=b$.
- *gt* indicates that $a>b$.
- *lt* indicates that $a<b$.

Problem information

Author : Jordi Cortadella

Generation : 2013-07-17 16:31:42

© Jutge.org, 2006–2013.

<http://www.jutge.org>