 

Circuit from state diagram

X76378_en

Design a sequential circuit described by the following state diagram.



The circuit has two inputs (x_1, x_0) and one output (z). The inputs can take the values 00, 01 and 10 (the value 11 will never occur and can be considered as a don't care).

Specification

```
module state_machine(x, z, clk, rst);  
    input [1:0] x;  
    input clk, rst;  
    output z;
```

Input

- clk is the clock signal.
- rst is the synchronous reset signal.
- x are the two input signals.

Output

- z is the output signal.

Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:58:11

© Jutge.org, 2006–2013.

<http://www.jutge.org>