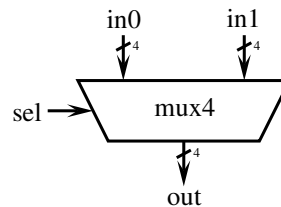

2-input multiplexer with 4-bit signals

X82780_en

Design a 2-input multiplexer in which the inputs are 4-bit wide. The selection signal is called *sel*, whereas the two inputs are called *in0* and *in1*. The output will be *in0* when *sel*=0 and *in1* when *sel*=1.

Specification

```
module mux4(in0, in1, sel, out);  
  input [3:0] in0, in1;  
  input sel;  
  output [3:0] out;
```



Input

- *in0* and *in1* are the two 4-bit inputs.
- *sel* is the selector.

Output

- *out* is the 4-bit output.

Problem information

Author : Javier de San Pedro Martín and Marta Miralpeix Anglerill

Generation : 2013-09-02 15:57:53

© Jutge.org, 2006–2013.

<http://www.jutge.org>