
n-bit adder

X84292_en

Design a circuit that performs the addition of two *n*-bit numbers. The result must be represented in *n* bits also. The number of bits *n* must be a parameter of the module.

Specification

```
module adder (a, b, cin, sum, cout);  
    parameter N=16;  
    input [N-1:0] a, b;  
    input cin;  
    output [N-1:0] sum;  
    output cout;
```

Hint

You may want to use several instances of a 1-bit full adder.

Input

- *a* and *b* are the two *n*-bit numbers.
- *cin* is the input carry.

Output

- *sum* is the *n*-bit output representing $(a + b) \bmod 2^n$.
- *cout* is the output carry.

Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:58:42

© Jutge.org, 2006–2013.

<http://www.jutge.org>