
***n*-bit adder/subtractor**

X89356_en

Design a circuit that performs the addition or subtraction of two n -bit numbers. The result (mod 2^n) must be represented in n bits also. The circuit has an input (op) that indicates which operation must be performed (0 for addition, 1 for subtraction).

The number of bits must be a parameter of the module, with a default value as shown in the specification.

Specification

```
module add_sub (a, b, op, result );
    parameter N=16;
    input [N-1:0] a, b;
    input op;
    output [N-1:0] result ;
```

Input

- a and b are the two n -bit operands.
- op indicates the type of operation (0 for addition, 1 for subtraction).

Output

- $result$ is the n -bit result of the operation (mod 2^n).

Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:58:47

© Jutge.org, 2006–2013.

<http://www.jutge.org>