
4-bit adder

X97441_en

Design a circuit that performs the addition of two 4-bit numbers. The result (mod 16) must be represented in 4 bits also.

Specification

```
module adder4(a, b, sum);  
    input [3:0] a, b;  
    output [3:0] sum;
```

Hint

You may want to use several instances of a 1-bit full adder.

Input

- a and b are the two 4-bit number.

Output

- sum is the 4-bit output representing $(a + b) \bmod 16$.

Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:56:50

© Jutge.org, 2006–2013.

<http://www.jutge.org>